

Opcode Decoder

Learning Objective

After this activity, you will be able to

- Design an opcode decoder using analytical digital design techniques, and
- Verify that the implementation you specify satisfies the requirements

Problem Statement

For this learning activity, you are **required** to design a digital decoding circuit to decode the 3-bit opcode for the instruction format shown in Figure 1. The 8 instructions are listed in Table 1.



Figure 1: Simple CPU Instruction Format

Table 1: Simple CPU Instructions

Opcode	Mnemonic	Operation
000	Load N	Load data register, D0, with the contents at memory address = N
001	Store N	Store contents of data register, D0, at memory address = N
010	Add N	The contents at memory address = N are added to the contents of data register, D0, and then stored in data register, D0
011	Sub N	The contents at memory address = N are subtracted from the contents of data register, D0, and then stored in data register, D0
100	Inc N	The contents at memory address = N are incremented by 1
101	Dec N	The contents at memory address = N are decremented by 1
110	Bra N	The Program Counter (PC) is loaded with the memory address = N
111	Beq N	The Program Counter (PC) is loaded with the memory address = N if the last arithmetic operation produced a result of zero (indicated by the zero bit of the ALU, Z = 1).

In order to verify your design, you will create a testbench similar to the one shown in Figure 2, which includes a **Test** component with an exhaustive set of input test vectors, shown in Figure 4, along with the results.

ECE2330 – Digital Logic Design

The **Execute** input is a signal generated by the Fetch-Execute Finite State Machine (FSM), which equals 0 when an instruction is being fetched and 1 when an instruction is being executed. Thus, the output that indicates which instruction to execute should equal 1 if and only if **Execute** = 1. Otherwise, if **Execute** = 0, they should all equal 0.

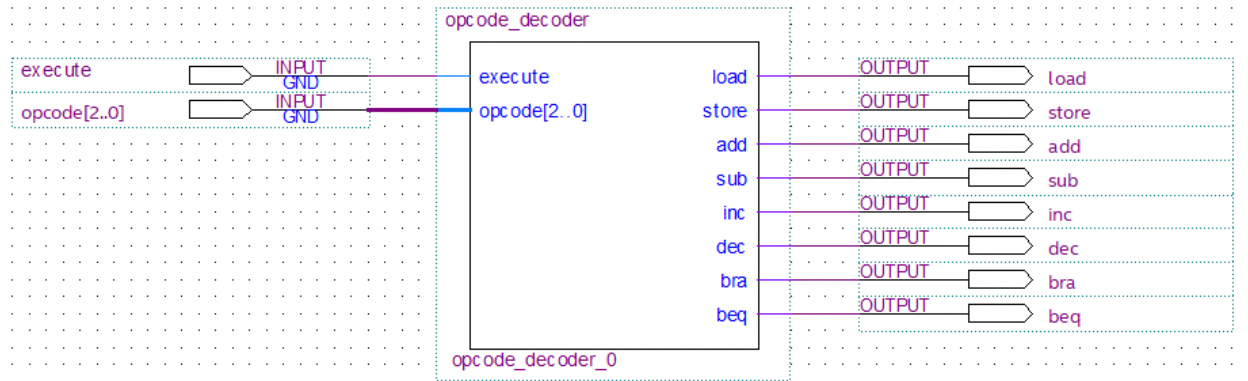


Figure 2: Opcode Decoder Testbench

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY opcode_decoder IS
    PORT
    (
        execute : IN  STD_LOGIC;
        opcode  : IN  STD_LOGIC_VECTOR(2 DOWNTO 0);
        load    : OUT STD_LOGIC;
        store   : OUT STD_LOGIC;
        add     : OUT STD_LOGIC;
        sub     : OUT STD_LOGIC;
        inc     : OUT STD_LOGIC;
        dec     : OUT STD_LOGIC;
        bra     : OUT STD_LOGIC;
        beq     : OUT STD_LOGIC
    );
END opcode_decoder;

```

Figure 3: VHDL Entity declaration for opcode decoder

 


Figure 4: Test Vectors and Results

ECE2330 – Digital Logic Design

What To Submit

You will submit the VHDL file you create as part of this assignment, along with simulation results for verification (as a PDF file, annotated appropriately where necessary).

Grading Rubric

This assignment is worth a total of 10 points:

- VHDL file of opcode decoder design
- VHDL file of testbench
- Numerical Verification