ECE2330 - Digital Logic Design

Simple Computer System

Learning Objective

After this activity, you will be able to

- Use a schematic capture tool to create a hierarchical design of a simple computer system,
- Verify that the implementation you specify satisfies the requirements, and
- Develop assembly programs to further verify your design

Problem Statement

For this learning activity, you are <u>required</u> to develop a hierarchical schematic of a simple computer system, as shown in Figure 1.

 


Figure 1: Simple Computer System Schematic

For this design, the **SimpleCPU** component is a hierarchical component that represents the Central Processing Unit (CPU) you have designed. You will verify the correct functionality of your design by loading the program shown in Figure 2 into the EEPROM. The program tests all 8 instructions, tests all components of **SimpleCPU**, and accesses almost every location in program/data memory.

The program is a self-modifying program, in that it modifies the instructions located at Memory Address (MA) 0x13 (dec 25) and 0x15 (inc 25) based on the value of **DataMemoryCounter** = 6 located at MA = 0x19.

The addresses of the two instructions that are modified are initialized with an address equal to **StartOfMemoryAddress** -1 = 25 (decimal), so that after modification the two instructions will decrement and increment the data at MA = 0x1F. Since this location is initialized with 0x00, the contents will change from 0x00 to 0xFF when decremented and then back to 0x00 when incremented.

Then, the modifications to the two instructions are reversed, **DataMemoryCounter** is decremented and tested for equality to zero.

If it is not equal to zero, the program branches to the beginning and repeats the process for the remaining data locations at MA = 0x1E down to 0x1B. If it is equal to zero, it is re-initialized with the value of **DataMemoryLength** (a constant), branches back to the beginning, and repeats the process.

ECE2330 - Digital Logic Design

You will be able to verify the correct design of your simple CPU if the program/data memory is essentially restored to its original state after all 6 data locations have been decremented/incremented and **DataMemoryCounter** has been re-initialized.

Memory Address	Memory Address	Data		Address	
(hex)	(decimal)	(Hex)	Instruction	(Decimal)	Description
00	0	19	load	25	load value of DataMemoryCounter
01	1	53	add	19	add value of DataMemoryCounter to instruction at MA = FunctionStartAddress
02	2	33	store	19	store modified instruction at MA = FunctionStartAddress
03	3	19	load	25	load value stored of DataMemoryCounter
04	4	55	add	21	add value of DataMemoryCounter to instruction at MA = FunctionStartAddress+2
05	5	35	store	21	store modified instruction at MA = FunctionStartAddress+2
06	6	D3	bra	19	branch to function at MA = FunctionStartAddress
07	7	13	load	19	load instruction stored at MA = FunctionStartAddress (reverse previous instruction effects)
08	8	79	sub	25	subtract value of DataMemoryCounter from instruction at MA = FunctionStartAddress
09	9	33	store	19	store modified instruction at MA = FunctionStartAddress
0A	10	15	load	21	load instruction stored at MA = FunctionStartAddress+2
OB	11	79	sub	25	subtract value of DataMemoryCounter from instruction at MA = FunctionStartAddress +2
0C	12	35	store	21	store modified instruction at MA = FunctionStartAddress+2
0D	13	В9	dec	25	decrement DataMemoryCounter
0E	14	F0	beq	16	if equal to zero, branch to MA = 16 to reset DataMemoryCounter with value = DataMemoryLength
0F	15	CO	bra	0	unconditional branch to MA = 0
10	16	18	load	24	load value of DataMemoryLength
11	17	39	store	25	store value of DataMemoryCounter
12	18	CO	bra	0	unconditional branch to MA = 0
13	19	В9	dec	25	FunctionStartAddress: Decrement value at MA (initial value of MA = StartOfDataMemory -1)
14	20	F7	beq	23	branch to MA = 23 if equal to zero (which should never occur)
15	21	99	inc	25	increment value at MA (initial value of MA = StartOfDataMemory -1)
16	22	E7	beq	7	branch to MA = 7 if equal to zero (which should always occur)
17	23	D7	bra	23	infinite loop - should never arrive here
18	24	6	data	6	DataMemoryLength (constant)
19	25	6	data	6	DataMemoryCounter variable location
1A	26	0	data	0	StartOfDataMemory
1B	27	0	data	0	
1C	28	0	data	0	
1D	29	0	data	0	
1E	30	0	data	0	
1F	31	0	data	0	

Figure 2: Simple CPU Test Program

Finally, you are <u>required</u> to develop a program to further test your design. The main program calls 4 functions sequentially, and then loops back to the beginning, looping indefinitely. The first function increments memory location 31 (hex = 1F) from 0 to **Limit** using the increment instruction, where **Limit** is a constant value stored as part of your program. The second function decrements memory location 31 from **Limit** to 0 using the decrement instruction.

The third function once again increments memory location 31 from 0 to **Limit**, but the addition instruction is used, and memory location 31 changes by **Delta**, where **Delta** is a constant value stored as part of your program. The fourth function once again decrements from **Limit** to 0 using the subtraction instruction and **Delta**. A flowchart of the required functionality is shown in Figure 3, and simulation results are shown in Figure 4, where **Limit** = 10 and **Delta** = 2.

ECE2330 - Digital Logic Design

 




Figure 4: Simulation results.

What To Submit

You will submit <u>all</u> VHDL files associated with the CPU design you created for this project. You will also submit an explanation of the program you wrote and simulation results for verification (as a PDF file, annotated appropriately where necessary).

Grading Rubric

This assignment is worth a total of 20 points:

- VHDL files of CPU design
- Required assembly program
- Numerical Verification